



# **AMD Summer Practice**

# **Implementarea**

# **MIPS**

# **în Verilog**

---

Proiect realizat de: Samachiş Eduard-Iulian

# MIPS – scurtă prezentare

---

# MIPS – scurtă prezentare

MIPS (Microprocessor without Interlocked Pipelined Stages) este un tip de arhitectură microprocesor, utilizată în special în sisteme embedded cum ar fi routerele, dispozitivele multimedia, senzorii și imprimantele.

Aceste procesoare sunt cunoscute pentru performanța lor ridicată la care se adaugă un consum mic de energie, rezultând o tehnologie eficientă din punct de vedere al costului.




# Implementare în Verilog



---

# Schema implementării

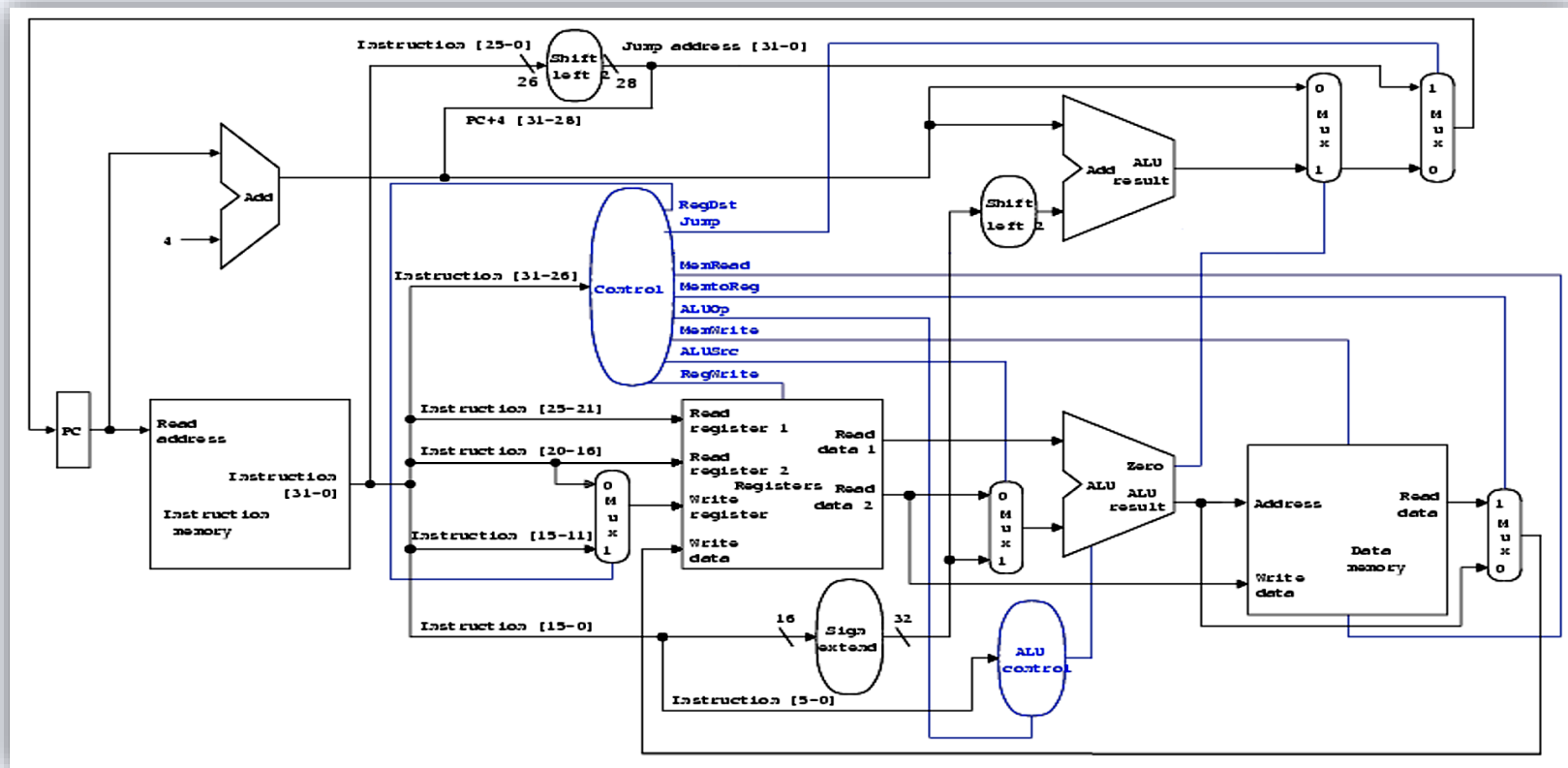

## Cod-ul implementării - modulele simple

```
module ProgramCounter(  
    input clk,  
    input [31:0] IN,  
    output reg [31:0] OUT = 0  
);  
  
    always@(posedge clk)  
        OUT <= IN;  
  
endmodule
```

```
module ADDER(  
    input [31:0] A,  
    input [31:0] B,  
    output [31:0] OUT  
);  
  
    assign OUT = A + B;  
  
endmodule
```

```
module SHL(  
    input [31:0] IN,  
    output [31:0] OUT  
);  
  
    assign OUT = IN << 2;  
  
endmodule
```

```
module MUX21#(parameter SIZE = 32) (  
    input [SIZE-1:0] IN0,  
    input [SIZE-1:0] IN1,  
    input SEL,  
    output [SIZE-1:0] OUT  
);  
  
    assign OUT = (SEL == 0) ? IN0 : IN1;  
  
endmodule
```

```
module SignExt(  
    input [15:0] IN,  
    input EXTOP, // sign extension bit  
    output [31:0] OUT  
);  
  
    assign OUT = {{16{EXTOP}}, IN};  
  
endmodule
```

## Cod-ul implementării - unitatea aritmetico-logică

```
module ALU(  
    input [31:0] A,  
    input [31:0] B,  
    input [3:0] OP,  
    output reg ZERO,  
    output reg [31:0] OUT  
);  
  
    always@({A,B,OP})  
    begin  
        case(OP)  
            4'b0000: begin OUT = A & B; ZERO = 0; end  
            4'b0001: begin OUT = A | B; ZERO = 0; end  
            4'b0010: begin OUT = A + B; ZERO = 0; end  
            4'b0110: begin OUT = A - B; ZERO = 0; end  
            4'b0111: {OUT,ZERO} = (A < B) ? 33'h0003 : 33'b0;  
            4'b1100: begin OUT = ~ ( A | B ); ZERO = 0; end  
            4'b0101: ZERO = (A == B) ? 1'b1 : 1'b0;  
        endcase  
    end  
endmodule
```

## Cod-ul implementării - instruction memory

```
module InstructionMemory( // Contains the program to be executed
    input [7:0] ADDRESS,
    output [31:0] INSTRUCTION
);
    reg [7:0] IM [99:0];

    initial
        $readmemb("InstrMem.mem", IM);

    assign INSTRUCTION = {IM[ADDRESS], IM[ADDRESS+1], IM[ADDRESS+2], IM[ADDRESS+3]};
endmodule
```



# Cod-ul implementării - registers bank

```
module RegisterBank(  
    input clk,  
    input RegWrite, // 1 if a register should be written  
    input [4:0] RA1, // read address  
    input [4:0] RA2,  
    input [4:0] WA, // write address  
    input [31:0] WD, // write data  
    output [31:0] RD1,  
    output [31:0] RD2  
);  
  
    reg [31:0] REGISTERS [31:0];  
  
    initial  
        $readmemh("MEM_INIT.mem", REGISTERS);  
  
    always@(posedge clk)  
        if(RegWrite)  
            REGISTERS[WA] <= WD;  
  
    assign RD1 = REGISTERS[RA1];  
    assign RD2 = REGISTERS[RA2];  
  
endmodule
```

REGISTERS[0] -> zero	REGISTERS[16] -> t8
REGISTERS[1] -> at	REGISTERS[17] -> t9
REGISTERS[2] -> v0	REGISTERS[18] -> s0
REGISTERS[3] -> v1	REGISTERS[19] -> s1
REGISTERS[4] -> a0	REGISTERS[20] -> s2
REGISTERS[5] -> a1	REGISTERS[21] -> s3
REGISTERS[6] -> a2	REGISTERS[22] -> s4
REGISTERS[7] -> a3	REGISTERS[23] -> s5
REGISTERS[8] -> t0	REGISTERS[24] -> s6
REGISTERS[9] -> t1	REGISTERS[25] -> s7
REGISTERS[10] -> t2	REGISTERS[26] -> k0
REGISTERS[11] -> t3	REGISTERS[27] -> k1
REGISTERS[12] -> t4	REGISTERS[28] -> gp
REGISTERS[13] -> t5	REGISTERS[29] -> sp
REGISTERS[14] -> t6	REGISTERS[30] -> fp
REGISTERS[15] -> t7	REGISTERS[31] -> ra

## Cod-ul implementării - data memory

```
module DataMemory( // RAM
    input clk,
    input MemWrite, // R-1    W-0
    input [31:0] WD, // write data - what we write to an address
    input [31:0] ADDR,
    output reg [31:0] RD, // read data - what we're reading from an address
    // for user
    input [11:0] data_in,
    output [11:0] data_read
);
    reg [31:0] ram [31:0];

    parameter MAX_ADDR = 32;

    initial
        $readmemh("MEM_INIT.mem", ram);

    always@(posedge clk) begin
        if(ADDR <= MAX_ADDR - 1) begin
            if(MemWrite)
                ram[ADDR] <= WD;
            else
                RD <= ram[ADDR];
        end

        ram[16] <= {20'b0,data_in};

    end

    assign data_read = ram[31][11:0];
endmodule
```

# Cod-ul implementării - unitatea de control

```
module ControlUnit(
    input [5:0] FUNCT,
    input [5:0] OPCODE,
    input ZERO, // from ALU
    output reg REG_DST, // 1 - select rd as destination register
    output reg REG_WRITE, // 1- activate the writing to the register
    output reg EX_TOP,
    output reg ALU_SRC, // 1 - immediate    0 - register
    output reg [3:0] ALU_OP, // ALU operation
    output reg MEM_WRITE, // 1 - write to memory
    output reg MEM2REG, // 0 - output comes from ALU    1 - output comes from data memory
    output reg PC_SRC, // PC_SRC = ZERO    0 - continues to PC+4    1 - branches to PC+4+(offset*4)
    output reg JUMP // jump to given address
);


always@(FUNCT or OPCODE or ZERO)
if(OPCODE == 6'b0) begin// R-TYPE
    case(FUNCT) // opcode (6) | r1 (5) | r2 (5) | rd (5) | shamt (5) | funct (6)
        6'b100_000 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0010_0_0; // add
        6'b100_010 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0110_0_0; // sub
        6'b100_100 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0000_0_0; // and
        6'b100_101 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0001_0_0; // or
        6'b101_010 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0111_0_0; // slt
        default : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b0;
    endcase
    {PC_SRC, JUMP} = 0;
end
```

# Cod-ul implementării - unitatea de control

```
else begin // I-TYPE and others
    casex(OPCODE)
        // I-TYPE -> opcode (6) rs (5) rd (5) offset (16)
        6'b001_000: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_1_0_1_0010_0_0_0_0; // addi
        //opcode (6) rs (5) rd (5) offset (16)
        6'b100_011: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_1_0_1_0010_0_1_0_0; // lw
        6'b101_011: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_0_0_1_0010_1_0_0_0; // sw
        6'b000_100: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, JUMP, PC_SRC} = {11'b0_0_1_0_0000_1_0_0, ZERO}; // beq
        // opcode (6) target (26)
        6'b000010: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_0_0_0_0000_0_1_0_1; // j
        default : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0;
    endcase
end

endmodule
```
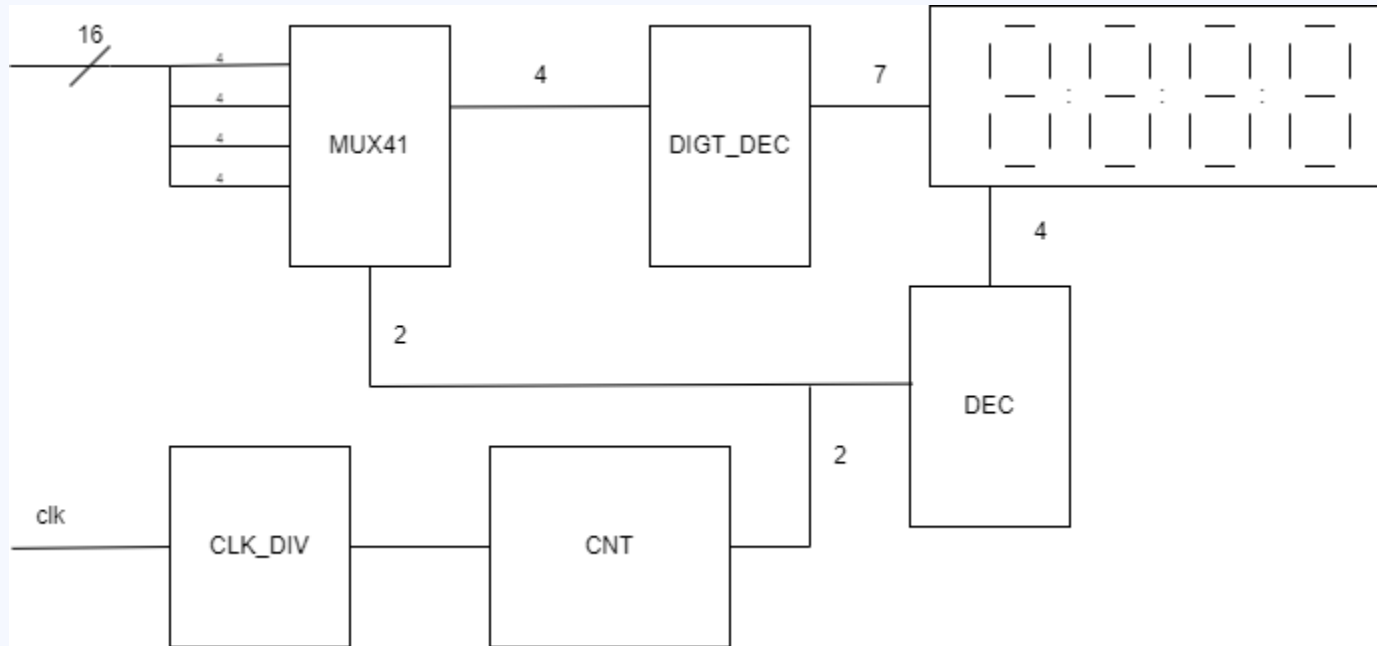
## Cod-ul implementării - afișarea pe display



# Cod-ul implementării - afișarea pe display

```
module clk_divider(clk, clk_out);
    input clk;
    output reg clk_out;

    parameter di = 138_875; // 33.33 Mhz / 240 hz -> clk_out = 240 hz
    reg[31:0] counter;

    initial begin
        counter <= 0;
        clk_out <= 0;
    end

    always@(posedge clk)
    begin
        if(counter >= di - 1)
        begin
            counter <= 0;
            clk_out <= ~clk_out;
        end
        else
            counter <= counter + 1;
        end
    end
endmodule
```

```
module DEC24(ain, aout);

    input [1:0] ain;
    output reg [3:0] aout;

    always@(ain) begin
        case(ain)
            2'b00: aout = ~4'b0001;
            2'b01: aout = ~4'b0010;
            2'b10: aout = ~4'b0100;
            2'b11: aout = ~4'b1000;
        endcase
    end
endmodule
```

```
module CNT2(clk, out);

    input clk;
    output reg [1:0] out;

    initial
        out <= 0;

    always@(posedge clk)
        if(out <= 2'b11) out <= out + 1;
        else out <= 0;

endmodule
```

```
module MUX41#(parameter SIZE = 4)(in3, in2, in1, in0, out, sel);
    input [SIZE-1:0] in0, in1, in2, in3;
    input [1:0] sel;
    output reg [SIZE-1:0] out;

    always@(sel)
        case(sel)
            0: out = in0;
            1: out = in1;
            2: out = in2;
            3: out = in3;
        endcase
endmodule
```

## Cod-ul implementării - afișarea pe display

```
module DIGT_DEC(in, a,b,c,d,e,f,g);
    input [3:0] in;
    output reg a, b, c, d, e, f, g;

    /*
        a
        -
    f | - | b
        - g
    e | - | c
        -
        d
    */

    always@(in)
        case(in)
            0: {a,b,c,d,e,f,g} <= ~ 7'b111_1110;
            1: {a,b,c,d,e,f,g} <= ~ 7'b011_0000;
            2: {a,b,c,d,e,f,g} <= ~ 7'b110_1101;
            3: {a,b,c,d,e,f,g} <= ~ 7'b111_1001;
            4: {a,b,c,d,e,f,g} <= ~ 7'b011_0011;
            5: {a,b,c,d,e,f,g} <= ~ 7'b101_1011;
            6: {a,b,c,d,e,f,g} <= ~ 7'b101_1111;
            7: {a,b,c,d,e,f,g} <= ~ 7'b111_0000;
            8: {a,b,c,d,e,f,g} <= ~ 7'b111_1111;
            9: {a,b,c,d,e,f,g} <= ~ 7'b111_1011;
            10: {a,b,c,d,e,f,g} <= ~ 7'b111_0111;
            11: {a,b,c,d,e,f,g} <= ~ 7'b001_1111;
            12: {a,b,c,d,e,f,g} <= ~ 7'b100_1110;
            13: {a,b,c,d,e,f,g} <= ~ 7'b011_1101;
            14: {a,b,c,d,e,f,g} <= ~ 7'b100_1111;
            15: {a,b,c,d,e,f,g} <= ~ 7'b100_0111;
            default: {a,b,c,d,e,f,g} <= ~ 7'b000_0001;
        endcase
endmodule
```

# Modulul TOP

```
module top(  
    input clk,  
    input [11:0] data_in_user  
);  
    wire [11:0] data_read_user;  
  
    // Display  
    wire clk_div;  
    wire [1:0] counter_out;  
    wire [3:0] mux_disp_out, dec_out;  
    wire a, b, c, d, e, f, g;  
  
    wire [31:0] PC_OUT, ADDER4_OUT, ADDER_SE_OUT, IM_OUT, RD1, RD2,  
                WD, SE_OUT, MUX2_OUT, ALU_OUT, RD, SHL2_OUT, MUX_PC_OUT, MUX_JUMP_OUT;  
  
    wire [4:0] MUX1_OUT;  
    wire [3:0] ALU_OP;  
  
    wire REG_DST, REG_WRITE, EX_TOP, ALU_SRC,  
        MEM_WRITE, MEM2REG, ZERO, PC_SRC, JUMP;  
  
    wire [5:0] FUNC, OPCODE;  
    wire [4:0] RA1, RA2, DestReg;  
    wire [25:0] JUMP_INSTR;  
  
    assign OPCODE = IM_OUT[31:26];  
    assign FUNC = IM_OUT[5:0];  
  
    assign RA1 = IM_OUT[25:21];  
    assign RA2 = IM_OUT[20:16];  
  
    assign DestReg = IM_OUT[15:11];  
    assign JUMP_INSTR = IM_OUT[25:0];
```



# Modulul TOP

```
ControlUnit CU(FUNC, OPCODE, ZERO,  
              REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP);  
  
ProgramCounter PC(clk, MUX_JUMP_OUT, PC_OUT);  
  
ADDER SUM4(PC_OUT, 32'h0000_0004, ADDER4_OUT);  
  
SHL shl1(SE_OUT, SHL2_OUT);  
  
ADDER SUM_SE(SHL2_OUT, ADDER4_OUT, ADDER_SE_OUT);  
  
MUX21#(32) mux_jump(MUX_PC_OUT, {ADDER_SE_OUT[31:28], JUMP_INSTR, 2'b0}, JUMP, MUX_JUMP_OUT);  
  
MUX21#(32) mux_pc(ADDER4_OUT, ADDER_SE_OUT, PC_SRC, MUX_PC_OUT);  
// PC_SRC 1 - Branches to PC+4+(offset*4)  
// PC_SRC 0 - continues to PC+4  
InstructionMemory IM(PC_OUT[7:0], IM_OUT);  
  
MUX21#(5) mux1(RA2, DestReg, REG_DST, MUX1_OUT);  
  
RegisterBank RegBank(clk, REG_WRITE, RA1, RA2, MUX1_OUT, WD, RD1, RD2);  
  
SignExt SE(IM_OUT[15:0], EX_TOP, SE_OUT); // ALU accepts either an operand, either a sign-extended immediate operand (lw, sw)  
  
MUX21#(32) mux2(RD2, SE_OUT, ALU_SRC, MUX2_OUT); // 0 - register operand    1 - immediate operand  
  
ALU alu(RD1, MUX2_OUT, ALU_OP, ZERO, ALU_OUT);  
//                               WD    ADDR    RD  
DataMemory DM(clk, MEM_WRITE, RD2, ALU_OUT, RD,  
              data_in_user, data_read_user  
              );  
  
MUX21#(32) mux3(ALU_OUT, RD, MEM2REG, WD);  
  
clk_divider div(clk, clk_div);  
  
CNT2 cnt(clk, counter_out);  
  
MUX41 disp_mux(4'b0, data_read_user[11:8], data_read_user[7:4], data_read_user[3:0],  
              mux_disp_out, counter_out);  
  
DEC24 dec24(counter_out, dec_out);  
  
DIGT_DEC digtdec(mux_disp_out, a, b, c, d, e, f, g);
```

## Modulul de test

```
module tb;
    reg clk;
    reg [11:0] data_in;
    top inst(clk, data_in);

    initial
    begin
        #0 clk = 0; data_in = 0;
        forever #5 clk = ~clk;
    end

    initial
        #120 $finish;

    initial
    begin
        forever #10 data_in = data_in + 1;
    end
endmodule
```

# Program de test

**addi x1, x1, 30**

001000\_00001\_00001\_0000\_0000\_0001\_1110

**addi x2, x2, 10**

001000\_00010\_00010\_0000\_0000\_0000\_1010

**add x3, x1, x2**

000000\_00001\_00010\_00011\_00000\_100000

**sub x3, x1, x2**

000000\_00001\_00010\_00011\_00000\_100010

**and x3, x1, x2**

000000\_00001\_00010\_00011\_00000\_100100

**or x3, x1, x2**

000000\_00001\_00010\_00011\_00000\_100101


**slt x3, x1, x2**

000000\_00010\_00001\_00011\_00000\_101010

**beq x3, x3, -8**

000100\_00011\_00011\_1111\_1111\_1111\_1000

# Test bench

 

# I0 mapping

**addi x0, x0, 16**

001000\_00000\_00000\_0000\_0000\_0001\_0000

**addi x2, x2, 31**

001000\_00010\_00010\_0000\_0000\_0001\_1111

**lw x1, 0(x0)**

100011\_00000\_00001\_0000\_0000\_0000\_0000


**sw x1, 0(x2)**

101011\_00\_010\_00001\_0000\_0000\_0000\_0000

**j 2**

000010\_00\_0000\_0000\_0000\_0000\_0000\_0010

# Test bench

 

# Concluzii





**Mulțumesc pentru  
atenție!**