



AMD Summer Practice

Implementarea

MIPS

în Verilog

Proiect realizat de: Samachiş Eduard-Iulian

MIPS – scurtă prezentare

MIPS – scurtă prezentare

MIPS (Microprocessor without Interlocked Pipelined Stages) este un tip de arhitectură microprocesor, utilizată în special în sisteme embedded cum ar fi routerele, dispozitivele multimedia, senzorii și imprimantele.


Aceste procesoare sunt cunoscute pentru performanța lor ridicată la care se adaugă un consum mic de energie, rezultând o tehnologie eficientă din punct de vedere al costului.



Implementare în Verilog



Schema implementării

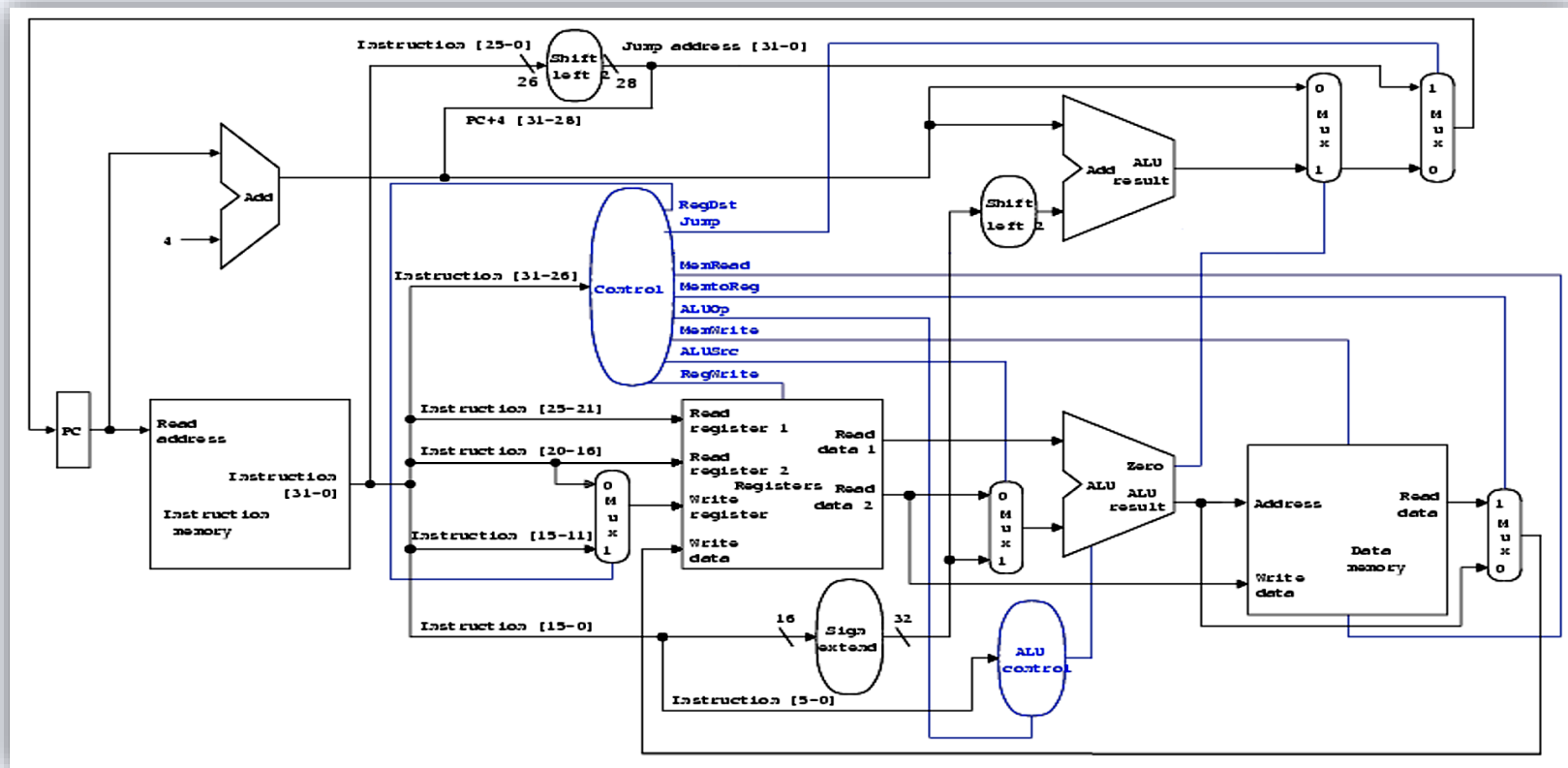

Cod-ul implementării - modulele simple

```
module ProgramCounter(  
    input clk,  
    input [31:0] IN,  
    output reg [31:0] OUT = 0  
);  
  
    always@(posedge clk)  
        OUT <= IN;  
  
endmodule
```

```
module ADDER(  
    input [31:0] A,  
    input [31:0] B,  
    output [31:0] OUT  
);  
  
    assign OUT = A + B;  
  
endmodule
```

```
module SHL(  
    input [31:0] IN,  
    output [31:0] OUT  
);  
  
    assign OUT = IN << 2;  
  
endmodule
```

```
module MUX21#(parameter SIZE = 32) (  
    input [SIZE-1:0] IN0,  
    input [SIZE-1:0] IN1,  
    input SEL,  
    output [SIZE-1:0] OUT  
);  
  
    assign OUT = (SEL == 0) ? IN0 : IN1;  
  
endmodule
```

```
module SignExt(  
    input [15:0] IN,  
    input EXTOP, // sign extension bit  
    output [31:0] OUT  
);  
  
    assign OUT = {{16{EXTOP}}, IN};  
  
endmodule
```

Cod-ul implementării - unitatea aritmetico-logică

```
module ALU(  
    input [31:0] A,  
    input [31:0] B,  
    input [3:0] OP,  
    output reg ZERO,  
    output reg [31:0] OUT  
);  
  
    always@({A,B,OP})  
    begin  
        case(OP)  
            4'b0000: begin OUT = A & B; ZERO = 0; end  
            4'b0001: begin OUT = A | B; ZERO = 0; end  
            4'b0010: begin OUT = A + B; ZERO = 0; end  
            4'b0110: begin OUT = A - B; ZERO = 0; end  
            4'b0111: {OUT,ZERO} = (A < B) ? 33'h0003 : 33'b0;  
            4'b1100: begin OUT = ~ ( A | B ); ZERO = 0; end  
            4'b0101: ZERO = (A == B) ? 1'b1 : 1'b0;  
        endcase  
    end  
endmodule
```

Cod-ul implementării - instruction memory

```
module InstructionMemory( // Contains the program to be executed
    input [7:0] ADDRESS,
    output [31:0] INSTRUCTION
);
    reg [7:0] IM [99:0];

    initial
        $readmemb("InstrMem.mem", IM);

    assign INSTRUCTION = {IM[ADDRESS], IM[ADDRESS+1], IM[ADDRESS+2], IM[ADDRESS+3]};
endmodule
```


Cod-ul implementării - registers bank

```
module RegisterBank(  
    input clk,  
    input RegWrite, // 1 if a register should be written  
    input [4:0] RA1, // read address  
    input [4:0] RA2,  
    input [4:0] WA, // write address  
    input [31:0] WD, // write data  
    output [31:0] RD1,  
    output [31:0] RD2  
);  
  
    reg [31:0] REGISTERS [31:0];  
  
    initial  
        $readmemh("MEM_INIT.mem", REGISTERS);  
  
    always@(posedge clk)  
        if(RegWrite)  
            REGISTERS[WA] <= WD;  
  
    assign RD1 = REGISTERS[RA1];  
    assign RD2 = REGISTERS[RA2];  
  
endmodule
```

REGISTERS[0] -> zero	REGISTERS[16] -> t8
REGISTERS[1] -> at	REGISTERS[17] -> t9
REGISTERS[2] -> v0	REGISTERS[18] -> s0
REGISTERS[3] -> v1	REGISTERS[19] -> s1
REGISTERS[4] -> a0	REGISTERS[20] -> s2
REGISTERS[5] -> a1	REGISTERS[21] -> s3
REGISTERS[6] -> a2	REGISTERS[22] -> s4
REGISTERS[7] -> a3	REGISTERS[23] -> s5
REGISTERS[8] -> t0	REGISTERS[24] -> s6
REGISTERS[9] -> t1	REGISTERS[25] -> s7
REGISTERS[10] -> t2	REGISTERS[26] -> k0
REGISTERS[11] -> t3	REGISTERS[27] -> k1
REGISTERS[12] -> t4	REGISTERS[28] -> gp
REGISTERS[13] -> t5	REGISTERS[29] -> sp
REGISTERS[14] -> t6	REGISTERS[30] -> fp
REGISTERS[15] -> t7	REGISTERS[31] -> ra

Cod-ul implementării - data memory

```
module DataMemory( // RAM
    input clk,
    input MemWrite, // R-1    W-0
    input [31:0] WD, // write data - what we write to an address
    input [31:0] ADDR,
    output reg [31:0] RD, // read data - what we're reading from an address
    // for user
    input [11:0] data_in,
    output [11:0] data_read
);
    reg [31:0] ram [31:0];

    parameter MAX_ADDR = 32;

    initial
        $readmemh("MEM_INIT.mem", ram);

    always@(posedge clk) begin
        if(ADDR <= MAX_ADDR - 1) begin
            if(MemWrite)
                ram[ADDR] <= WD;
            else
                RD <= ram[ADDR];
        end

        ram[16] <= {20'b0,data_in};
    end

    assign data_read = ram[31][11:0];
endmodule
```

Cod-ul implementării - unitatea de control

```
module ControlUnit(
    input [5:0] FUNCT,
    input [5:0] OPCODE,
    input ZERO, // from ALU
    output reg REG_DST, // 1 - select rd as destination register
    output reg REG_WRITE, // 1- activate the writing to the register
    output reg EX_TOP,
    output reg ALU_SRC, // 1 - immediate    0 - register
    output reg [3:0] ALU_OP, // ALU operation
    output reg MEM_WRITE, // 1 - write to memory
    output reg MEM2REG, // 0 - output comes from ALU    1 - output comes from data memory
    output reg PC_SRC, // PC_SRC = ZERO    0 - continues to PC+4    1 - branches to PC+4+(offset*4)
    output reg JUMP // jump to given address
);


always@(FUNCT or OPCODE or ZERO)
if(OPCODE == 6'b0) begin// R-TYPE
    case(FUNCT) // opcode (6) | r1 (5) | r2 (5) | rd (5) | shamt (5) | funct (6)
        6'b100_000 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0010_0_0; // add
        6'b100_010 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0110_0_0; // sub
        6'b100_100 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0000_0_0; // and
        6'b100_101 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0001_0_0; // or
        6'b101_010 : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b1_1_0_0_0111_0_0; // slt
        default : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG} = 10'b0;
    endcase
    {PC_SRC, JUMP} = 0;
end
```

Cod-ul implementării - unitatea de control

```
else begin // I-TYPE and others
    casex(OPCODE)
        // I-TYPE -> opcode (6) rs (5) rd (5) offset (16)
        6'b001_000: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_1_0_1_0010_0_0_0_0; // addi
        //opcode (6) rs (5) rd (5) offset (16)
        6'b100_011: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_1_0_1_0010_0_1_0_0; // lw
        6'b101_011: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_0_0_1_0010_1_0_0_0; // sw
        6'b000_100: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, JUMP, PC_SRC} = {11'b0_0_1_0_0000_1_0_0, ZERO}; // beq
        // opcode (6) target (26)
        6'b000010: {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0_0_0_0_0000_0_1_0_1; // j
        default : {REG_DST, REG_WRITE, EX_TOP, ALU_SRC, ALU_OP, MEM_WRITE, MEM2REG, PC_SRC, JUMP} = 12'b0;
    endcase
end

endmodule
```

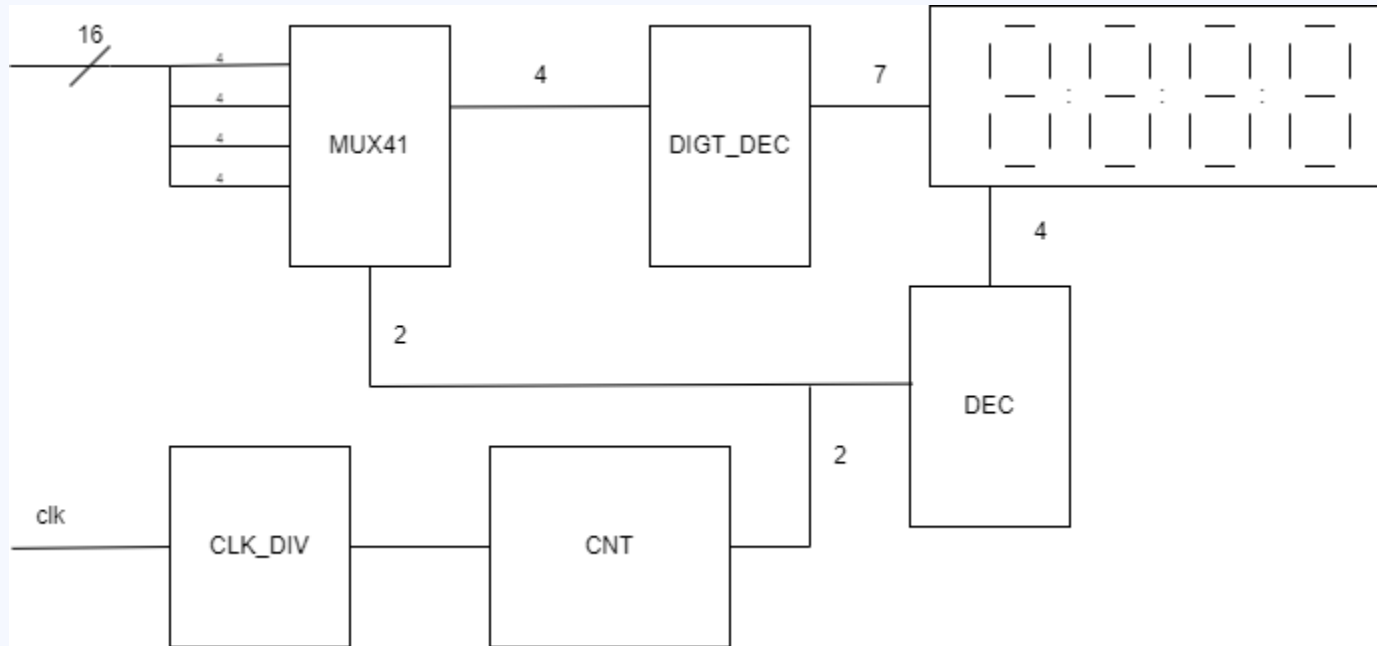Cod-ul implementării - afișarea pe display



Cod-ul implementării - afișarea pe display

```
module clk_divider(clk, clk_out);
    input clk;
    output reg clk_out;

    parameter di = 138_875; // 33.33 Mhz / 240 hz -> clk_out = 240 hz
    reg[31:0] counter;

    initial begin
        counter <= 0;
        clk_out <= 0;
    end

    always@(posedge clk)
    begin
        if(counter >= di - 1)
            begin
                counter <= 0;
                clk_out <= ~clk_out;
            end
        else
            counter <= counter + 1;
        end
    end
endmodule
```

```
module DEC24(ain, aout);

    input [1:0] ain;
    output reg [3:0] aout;

    always@(ain) begin
        case(ain)
            2'b00: aout = ~4'b0001;
            2'b01: aout = ~4'b0010;
            2'b10: aout = ~4'b0100;
            2'b11: aout = ~4'b1000;
        endcase
    end
endmodule
```

```
module CNT2(clk, out);

    input clk;
    output reg [1:0] out;

    initial
        out <= 0;

    always@(posedge clk)
        if(out <= 2'b11) out <= out + 1;
        else out <= 0;

endmodule
```

```
module MUX41#(parameter SIZE = 4)(in3, in2, in1, in0, out, sel);
    input [SIZE-1:0] in0, in1, in2, in3;
    input [1:0] sel;
    output reg [SIZE-1:0] out;

    always@(sel)
        case(sel)
            0: out = in0;
            1: out = in1;
            2: out = in2;
            3: out = in3;
        endcase
endmodule
```

Cod-ul implementării - afișarea pe display

```
module DIGT_DEC(in, a,b,c,d,e,f,g);
    input [3:0] in;
    output reg a, b, c, d, e, f, g;

    /*
        a
        -
    f | - | b
        - g
    e | - | c
        -
        d
    */

    always@(in)
        case(in)
            0: {a,b,c,d,e,f,g} <= ~ 7'b111_1110;
            1: {a,b,c,d,e,f,g} <= ~ 7'b011_0000;
            2: {a,b,c,d,e,f,g} <= ~ 7'b110_1101;
            3: {a,b,c,d,e,f,g} <= ~ 7'b111_1001;
            4: {a,b,c,d,e,f,g} <= ~ 7'b011_0011;
            5: {a,b,c,d,e,f,g} <= ~ 7'b101_1011;
            6: {a,b,c,d,e,f,g} <= ~ 7'b101_1111;
            7: {a,b,c,d,e,f,g} <= ~ 7'b111_0000;
            8: {a,b,c,d,e,f,g} <= ~ 7'b111_1111;
            9: {a,b,c,d,e,f,g} <= ~ 7'b111_1011;
            10: {a,b,c,d,e,f,g} <= ~ 7'b111_0111;
            11: {a,b,c,d,e,f,g} <= ~ 7'b001_1111;
            12: {a,b,c,d,e,f,g} <= ~ 7'b100_1110;
            13: {a,b,c,d,e,f,g} <= ~ 7'b011_1101;
            14: {a,b,c,d,e,f,g} <= ~ 7'b100_1111;
            15: {a,b,c,d,e,f,g} <= ~ 7'b100_0111;
            default: {a,b,c,d,e,f,g} <= ~ 7'b000_0001;
        endcase
endmodule
```

Program de test

addi x1, x1, 30

001000_00001_00001_0000_0000_0001_1110

addi x2, x2, 10

001000_00010_00010_0000_0000_0000_1010

add x3, x1, x2

000000_00001_00010_00011_00000_100000

sub x3, x1, x2

000000_00001_00010_00011_00000_100010

and x3, x1, x2

000000_00001_00010_00011_00000_100100

or x3, x1, x2

000000_00001_00010_00011_00000_100101


slt x3, x1, x2

000000_00010_00001_00011_00000_101010

beq x3, x3, -8

000100_00011_00011_1111_1111_1111_1000

Test bench

 

I0 mapping

addi x0, x0, 16

001000_00000_00000_0000_0000_0001_0000

addi x2, x2, 31

001000_00010_00010_0000_0000_0001_1111

lw x1, 0(x0)

100011_00000_00001_0000_0000_0000_0000


sw x1, 0(x2)

101011_00_010_00001_0000_0000_0000_0000

j 2

000010_00_0000_0000_0000_0000_0000_0010

Test bench

 



**Mulțumesc pentru
atenție!**